

# Electronics

(For Sixth Semester General Course)

## Lecture 4

Manoj Kr. Das  
Associate Professor  
Physics Department  
J N College, Boko

# Transistor:

A junction transistor is made up of a semiconductor such as *Ge* or *Si* in which a *P-type* thin layer is sandwiched between two *N-type* layers. The transistor so formed is called *N – P – N* transistor. Alternately a transistor can also have an *N-type* layer between two *P-type* layers. The transistor is then termed a *P – N – P* transistor. *P – N – P* and *N – P – N* transistor are systematically shown in *Fig 1* and *Fig 2*.

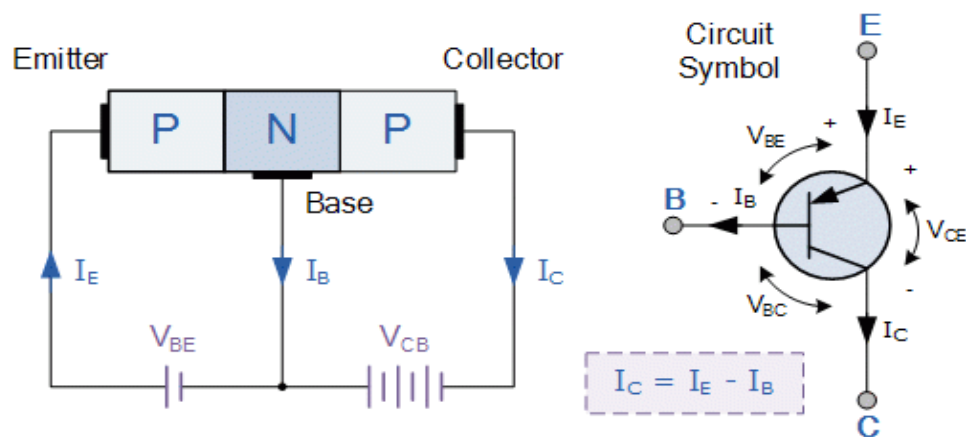


Fig 1

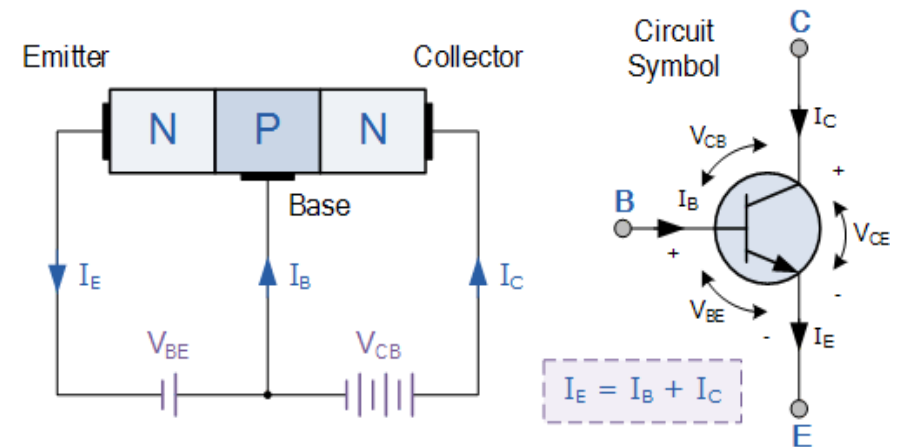


Fig 2

The middle portion of the transistor is called the Base and the two end portions are known as Emitter and Collector. The emitter-base junction is usually referred as emitter junction( $J_E$ ) and the collector-base junction as the collector junction( $J_C$ ). The size of the transistor is quite small. The structure is sealed inside a metal or plastic case to protect it from moisture. Metal leads *E, B and C* come out of the package for connection to the emitter, the base and the collector respectively. Since both the majority and minority carriers are involved in a junction transistor the device is termed as *bipolar junction transistor(BJT)*, *bipolar transistor* or *bipolar device*.

In the normal transistor operation emitter-base junction is forward biased and the collector-base junction is reversed biased. The current enters the transistor through the emitter terminal for a *P – N – P* transistor.

On the other hand current leaves the transistor through the for an  $N - P - N$  transistor. In both case the emitter, base and collector currents  $I_E$ ,  $I_B$  and  $I_C$  respectively are taken positive when the currents go into the transistor. The symbols  $V_{EB}$ ,  $V_{CB}$  and  $V_{CE}$  represent respectively the emitter-base, collector-base and collector-emitter voltages.

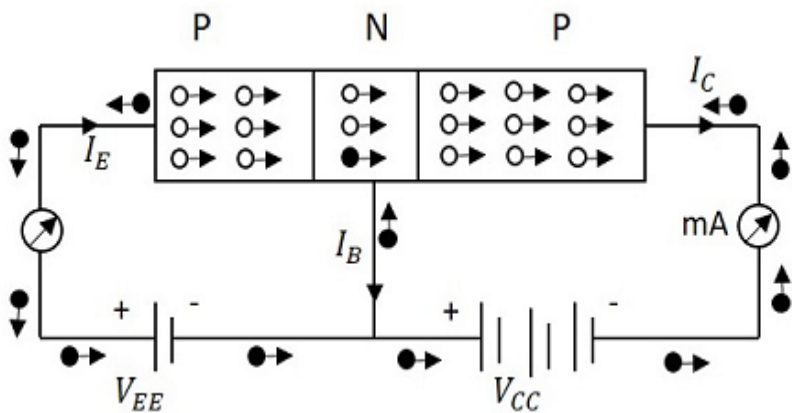


Fig 3

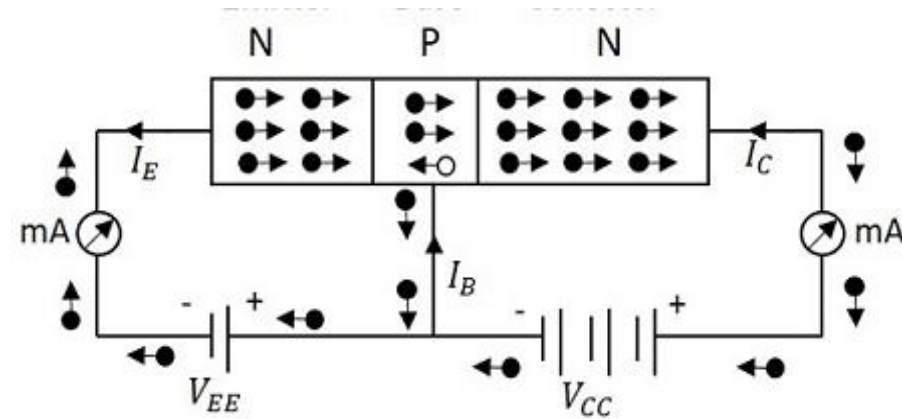


Fig 4

The operation of  $P - N - P$  transistor can be explained by *Fig 3*. Here emitter-base junction is forward biased and collector-base is in reversed biased. Hence voltage  $V_{EE}$  provides positive potential at the emitter which repel the holes in the  $P - type$  material and these holes cross the emitter-base junction to reach the base region. There a very low percent of holes recombine with free electrons of  $N-region$ . These provide a very low current which constitute the base current  $I_B$ . The remaining holes cross the collector-base junction to constitute the collector current  $I_C$  which is the hole current. As a hole reaches the collector terminal an electron from the battery negative terminal fills the space in collector. The flow slowly increases and the electron minority current flows through the emitter where each electron entering the positive terminal of  $V_{EE}$  is replaced by a hole by moving towards the emitter junction. This constitute emitter current  $I_E$ .

Three points are important for  $P - N - P$  transistor

- a) The conduction in  $P - N - P$  transistor takes place through holes.
- b) The collector current is slightly less than the emitter current
- c) The increase or decrease in emitter current affects the collector current.

Similarly the operation of  $N - P - N$  transistor can be explained by *Fig 4*, in which emitter-base junction forward biased and collector-base junction is reversed biased. The  $V_{EE}$  provides negative potential at the emitter which repels the electrons in the  $N - type$  material and these electrons cross the emitter-base junction to reach the base region. This flow slowly increases and the electron current flows through the transistor.

The points are important for  $N - P - N$  transistor

The conduction in a  $N - P - N$  transistor takes place through electrons.

The collector current is higher than the emitter current.

The increase or decrease in the emitter current affects the collector current.

The amplification factor  $\alpha$  and  $\beta$  may be defined as

$$\alpha = \left( \frac{\partial I_C}{\partial I_E} \right) \rightarrow (i), \text{ when } V_{CB} \text{ is constant}$$
$$\beta = \left( \frac{\partial I_C}{\partial I_B} \right) \rightarrow (ii), \text{ when } V_{CE} \text{ is constant}$$

By definition  $\Delta I_C = \alpha \cdot \Delta I_E$

The magnitude of emitter current is equal to sum of collector and base current. Thus

$$|\Delta I_E| = |\Delta I_C| + |\Delta I_B| = |\alpha I_E| + |\Delta I_B|$$

$$\Rightarrow \Delta I_B = \Delta I_E (1 - \alpha)$$

$$\Rightarrow \frac{\Delta I_B}{\Delta I_C} = \frac{\Delta I_E}{\Delta I_C} (1 - \alpha)$$

$$\Rightarrow \frac{1}{\beta} = \frac{1}{\alpha} (1 - \alpha)$$

$$\Rightarrow \beta = \frac{\alpha}{1 - \alpha} \rightarrow (iii)$$



The emitter current  $I_E$  consist of two component. One is hole component of emitter current  $I_{PE}$  and other is electron component of emitter current  $I_{NE}$ . The emitter efficiency ( $\gamma$ ) is defined as ratio of change in injected component of hole current  $I_{PE}$  to the total emitter current  $I_E$ .

Thus Emitter Efficiency

$$\gamma = \frac{\Delta I_{PE}}{\Delta I_E} = \frac{\Delta I_{PE}}{\Delta I_{PE} + \Delta I_{NE}} \rightarrow (iv)$$

The transport factor

$$\beta^* = \frac{\Delta I_C}{\Delta I_{PE}} \approx \frac{\Delta I_{PC}}{\Delta I_{PE}} \rightarrow (v)$$

$\beta^*$  will be high if highest possible amount of hole current reaches the collector junction, this will be available as collector current. The relation between  $\alpha$ ,  $\beta^*$  and  $\gamma$  are

$$\alpha = \frac{\Delta I_C}{\Delta I_E} = \left( \frac{\Delta I_C}{\Delta I_{PE}} \right) \cdot \left( \frac{\Delta I_{PE}}{\Delta I_E} \right) = \beta^* \cdot \gamma \rightarrow (vi)$$

The collector efficiency  $\delta$  is defined as the ratio of current leaving the collector region to the hole current entering the collector region from base.

### **Transistor Biasing:**

In transistor biasing amplifier, it is essential that the emitter-base junction should be forward biased and collector-base junction should be reversed biased. The circuit providing the desired biasing is known as biasing circuit.

The transistor biasing is defined as proper flow of zero signal of collector current and the maintenance of CE voltage during the passage of the signal. If transistor is not properly biased it works inefficiently and it gives distorted output signal. In addition amount of biased required is important for establishing  $Q - point$ . It is also important that  $Q - point$  should be stable. It means that  $Q - point$  should not shift due to rise of temperature.

### **Base Bias or Fixed Current Bias:**


A high resistance  $R_B$  is connected as shown in *Fig 5* The required zero signal base current is provided by  $V_{CC}$  which passes through  $R_B$ . By proper selection of  $R_B$  the required base current  $I_B$  can be made to flow.

Let  $I_C$  be required zero signal collector current.

$$V_{CC} = I_B R_B + V_{BE} \rightarrow (vii)$$

$$\Rightarrow R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{V_{CC}}{I_B} \rightarrow (viii)$$

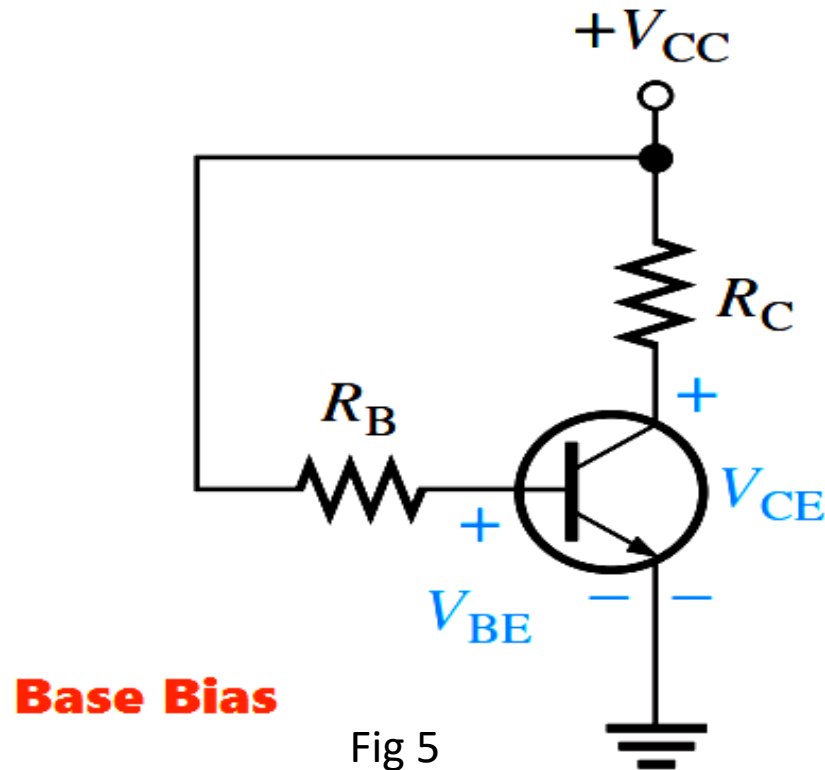Here  $V_{BE}$  is very small so can be negligible.



## Base biased with Emitter Feedback:

Here only an emitter resistor is connected to the base circuit.  
At saturation  $V_{CC}$  is essentially zero.

The saturated collector current is

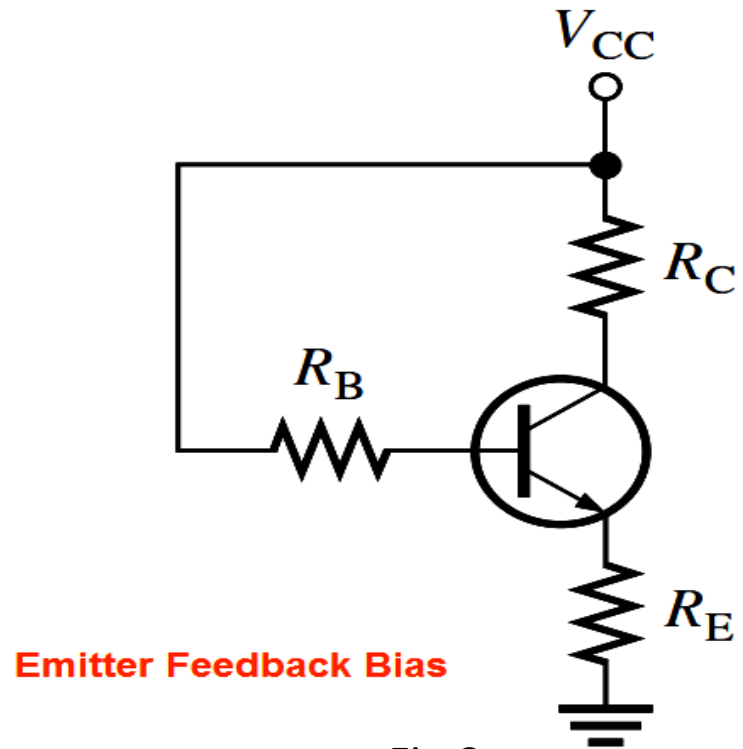


Fig 6

This increase in base voltage reduce the voltage across  $R_B$ , thus reducing the base current and keeping the collector current from increasing. A similar action occurs if the collector current tries to decrease. While this is better for linear circuit than base bias, it is still dependent on  $\beta$  and is not predictable as voltage divider bias.

### **Base Bias with Collector Feedback:**

Here one end of  $R_B$  is connected to base while other end is connected to collector. Here zero signal base current is determined by  $V_{CB}$  and it is forward bias the base-emitter junction and  $I_B$  flows  $R_B$ . This causes zero signal collector current to flow in the circuit.

Here voltage for  $R_B$  is derived from the collector, there exist a negative feed back effect which stabilized  $I_C$  against changes in  $\beta$ . Here  $R_B$  is connected to the collector rather than  $V_{CC}$ . The collector voltage provides bias for base-emitter junction. The negative feedback creates an offsetting effect that tends to keep the  $Q - point$  stable.

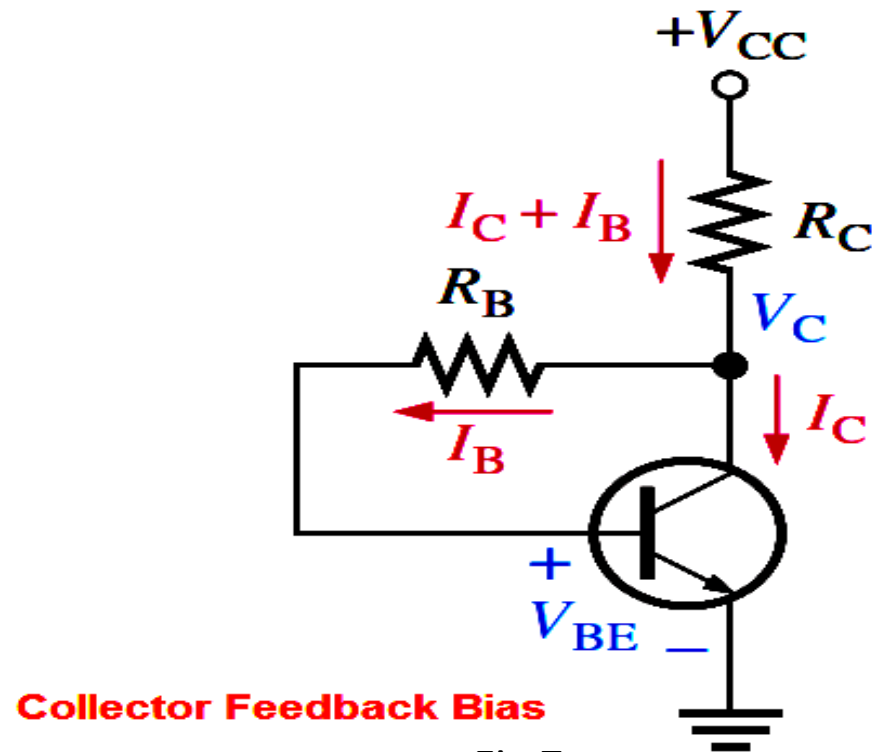


Fig 7

If  $I_C$  tends to increase it drops more voltage across  $R_C$  thereby causing  $V_C$  to decrease. When  $V_C$  decreases there is decrease in voltage across  $R_B$ , which decreases  $I_B$ . The decrease in  $I_B$  produces less  $I_C$  which in turn drops less voltage across  $R_C$  and thus offsets the decrease in  $V_C$ .

Here, since the emitter is grounded  $V_{CE} = V_C$

$$V_{CE} = V_{CC} - I_C R_C \rightarrow (ix)$$

This does not provide good stabilization.



## Base Bias with Collector and Emitter feedback:

Better stabilization of  $Q - point$  may be achieved by base bias with emitter and collector feed back as shown in Fig 8. Here when  $\beta$  increases emitter voltage increases but collector voltage decrease. So that voltage across  $R_B$  reduces which causes  $I_B$  to decrease

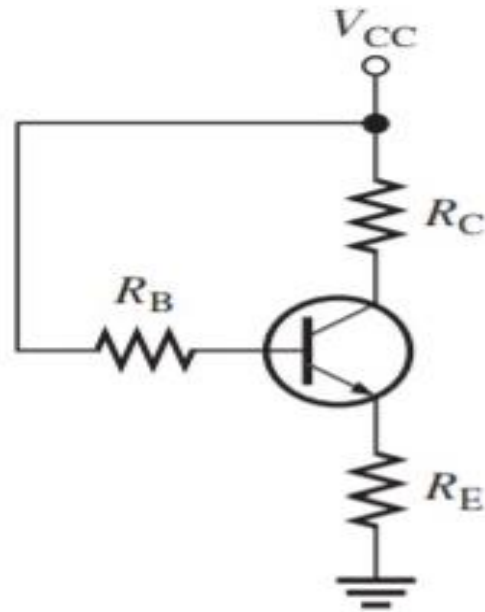


Fig 8

$$(I_C)_{saturated} = \frac{V_{CC}}{R_C + R_E}$$

Here  $I_B \approx \textit{small}$  . Therefore we have

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_E + \frac{R_B}{\beta}} \rightarrow (x)$$

### **Voltage Divider or Self Bias:**

Here two resistance  $R_1$  and  $R_2$  are connected across the supply voltage  $V_{CC}$ . The emitter resistance  $R_E$  provides the stabilization. The voltage divider is derived from the fact that resistance  $R_1$  and  $R_2$  form a potential divider across the  $V_{CC}$ .

The voltage drop across  $R_2$  forward biased the base-emitter junction while  $V_{CC}$  supply reverse biased the base-collector junction. The forward bias on base-emitter junction causes the base current and hence collector current flows in zero signal condition

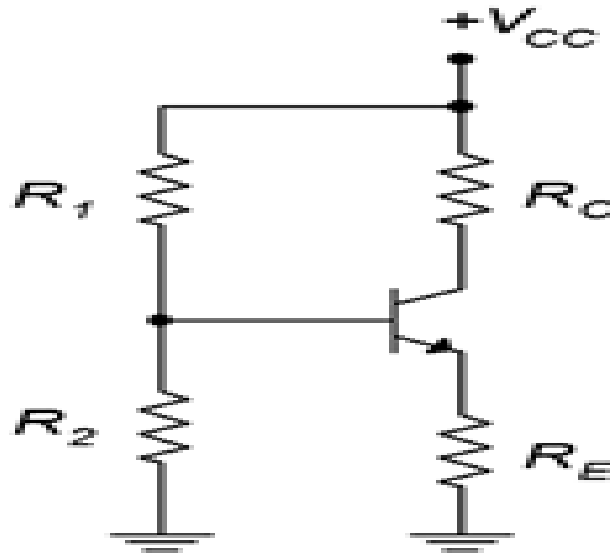


Fig 9

Voltage divider bias is the most popular and used may to bias a transistor. It uses few resistors to make sure that a voltage is divided and distributed into the transistor at correct levels. One resistor, the emitter resistor also helps to provide stability against variation in  $\beta$  may exist from transistor to transistor. Here stability is good. In this case  $I_C$  tend to increase due to increase *in*  $I_{CO}$  (leakage current) because of temperature rise. This increase current  $I_C$  cases an increase DC voltage drop across  $R_E$ . This reduces net emitter to base forward bias. As a result the base current  $I_B$  is reduced. The reduction in the base current causes a reduction in collector current. Thus the self biasing resistor  $R_E$  reduces the increase in  $I_C$  and improves the operating point stability.